

Cookie Making Machine Controller

a convyer belt



3 sensors: $S_0=1$, if cookie is burned
 $S_1=1$, if cookie too light
 $S_2=1$, if cookie not round



- want to reject the cookie if any two sensors = 1
- make a signal $R=1$ if any two or more sensors = 1
- if cookie is ok, need to wrap it. \rightarrow set an output $Wrap=1$. it takes 2 cycle to wrap.
 not ok, set $Done=1$ & it will be rejected.

*: machines run when $Run=1$ & doesn't when $Run=0$

*: release cookie for analysis by sensors

\Rightarrow - A FSM has several states:


we know what state we are in because an n-bit registers tells us what state we're in

- In each state we do 2 things:

①. Set specific output signals

②. Determine the next state based on the inputs and the current state

- Digital Hardware for this machine

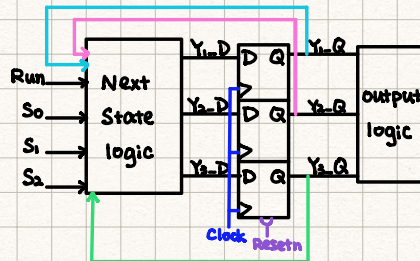

- Describe states & State diagram

T_0 : reset state, wait for $Run=1 \rightarrow New=1$

T_1 : wait for sensors to sense

T_2 : determine if cookie is OK

T_3 : 1st wrap cycle

T_4 : 2nd wrap cycle

